
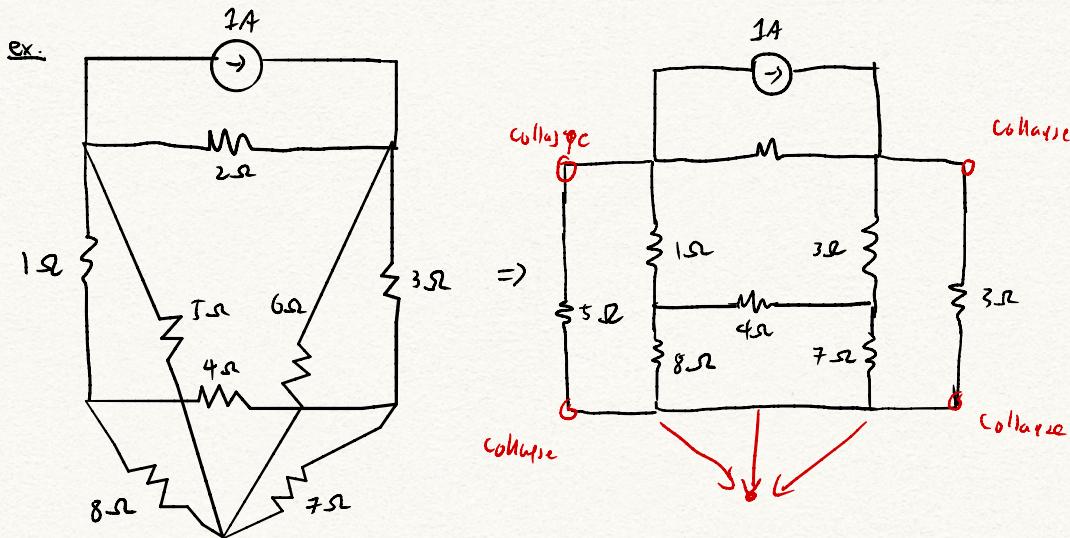



MESH ANALYSIS

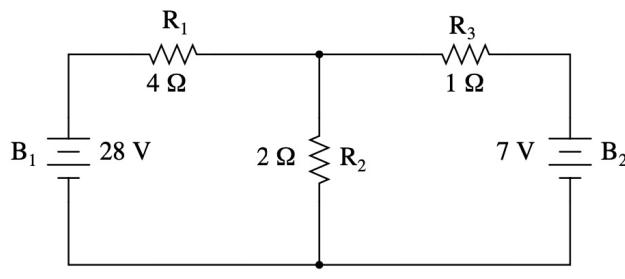- does not use KCL, can solve w/ less variables & less eqns.
- uses KVL to find currents, whereas Nodal Analysis uses KCL to find voltages.
- only works on **planar** circuits
- planar circuit \Rightarrow one that can be drawn in plane w/ no branches crossing e.g.
 \hookrightarrow a circuit that is initially, nonplanar might still work, if it can be redrawn as planar.






1. Identify loops

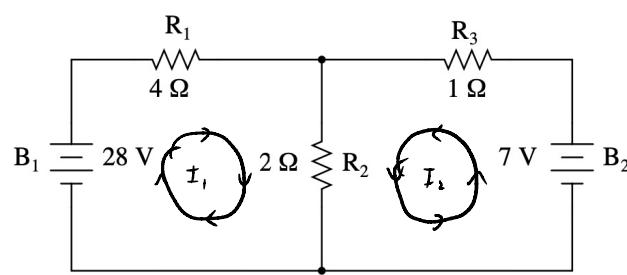

- gets its name by thinking of current loops like spinning gears.
- choice of current is arbitrary, but easier to solve if going thru same direction via intersecting components

2. Label voltage drop polarities

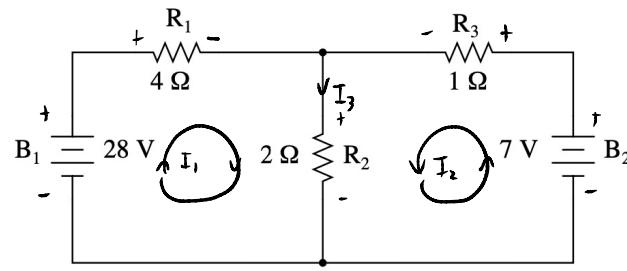

3. Write KVL for each loop

$$-28 + 4I_1 + 2(I_1 + I_2) = 0$$

$$-7 + I_2 + 2(I_1 + I_2) = 0$$


4. Solve for currents

$$I_1 = 5 \text{ A}$$

$$I_2 = -1 \text{ A}$$

$$I_3 = I_1 + I_2 = 4 \text{ A}$$

Ex.

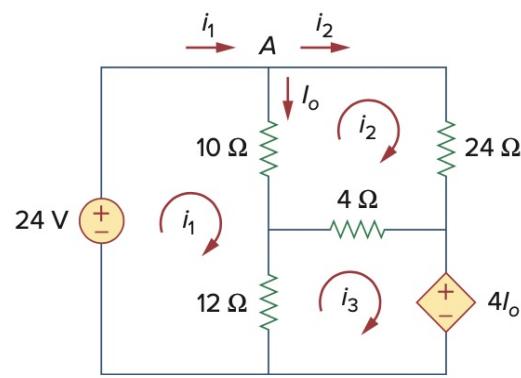

At don't assign
problem!!

$$10 + 4 + 24 = \\ |4 = 32$$

$$24 = 10(I_1 - I_2) + 12(I_1 - I_3)$$

$$0 = 24I_2 + 4(I_2 - I_3) + 10(I_2 - I_1)$$

$$4I_o + 12(I_3 - I_1) + 4(I_3 - I_2) = 0$$

$$I_o = I_1 - I_2$$

$$\Rightarrow 4(I_1 - I_2) + 12(I_3 - I_1) + 4(I_3 - I_2) = 0$$

$$-4 -4$$

$$\begin{aligned} 22I_1 - 10I_2 - 12I_3 &= 24 \\ -10I_1 + 38I_2 - 4I_3 &= 0 \\ -8I_1 - 8I_2 + 16I_3 &= 0 \end{aligned}$$

$$I_1 = 2.25 \text{ A}$$


$$I_2 = 0.75 \text{ A}$$

$$I_3 = 1.5 \text{ A}$$

$$I_o = 1.5 \text{ A}$$

WITH CURRENT SOURCES

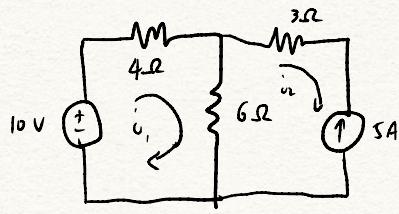- If current source exists only in one mesh




$$i_2 = -5 \text{ A}$$

$$i_0 = 4i_1 + 6(i_1 - i_2)$$


$$i_0 = 10i_1 - 6i_2$$

$$i_1 = \frac{10 + 6(-5)}{10} = -2 \text{ A}$$

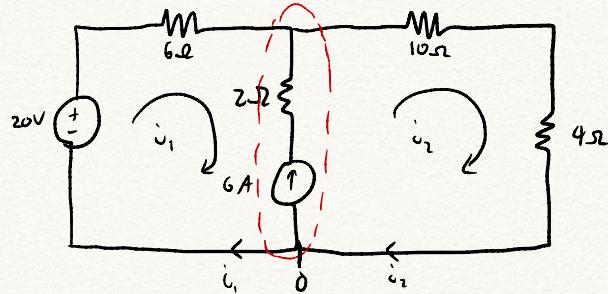- if current source between two meshes, create supermesh



↳ we ignore & run KVL on outer loop

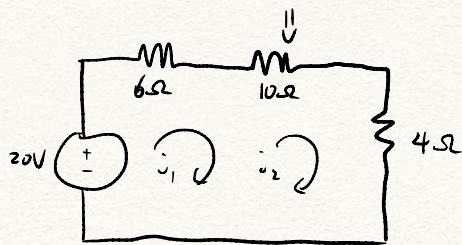

$$20 = 6i_1 + 10i_2 + 4i_3 \quad (\text{KVL})$$

$$10 = 3i_1 + 7i_2$$

Apply KCL to node in branch where two meshes intersect.

at node 0!

$$i_3 = 6 + i_1$$

$$10 = 3i_1 + 7(6 + i_1)$$


$$10 = 10i_1 + 42$$

$$i_1 = \frac{-32}{10} = -\frac{16}{5} = -3.2A$$

$$i_2 = 2.8A$$

Properties

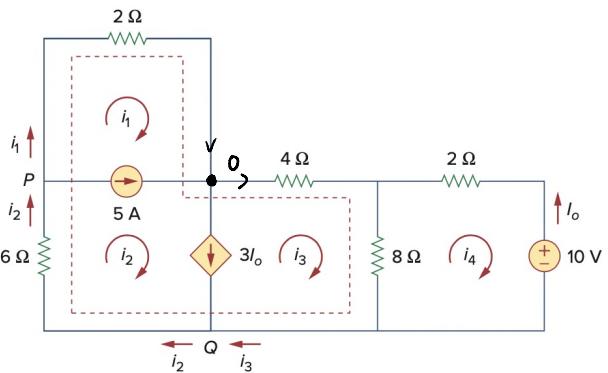- current source in supermesh gives eqn. to side current
- supermesh has no current of its own
- supermesh requires application of KCL & KVL.



KVL on larger supermesh

$$2i_1 + 4i_3 + 8(i_3 - i_4) + 6i_2 = 0 \quad i_1 = -7.5A$$

$$i_1 + 3i_2 + 6i_3 - 4i_4 = 0 \quad i_2 = -2.5A$$

at point P:

$$v_2 = i_1 + 5 \quad -i_1 + i_2 = 5 \quad i_3 = 3.93A$$

at point Q:

$$3I_o + i_3 = v_2 \quad -i_1 + i_2 = 5 \quad i_4 = 2.14A$$

at point O:

$$-3i_4 + i_3 = v_2 \Rightarrow i_2 - i_3 + 3i_4 = 0$$


at point O' :

$$5 + i_1 = 3I_o + i_3 \quad \text{in mesh 4:} \quad 10 + 8(i_4 - i_3) + 2i_4 = 0$$

$$I_o = -i_4 \quad 10 = 8i_3 - 10i_4$$

$$5 + i_1 = -3i_4 + i_3 \quad 5 = 4i_3 - 5i_4$$


NODAL / MESH ANALYSIS BY INSPECTION

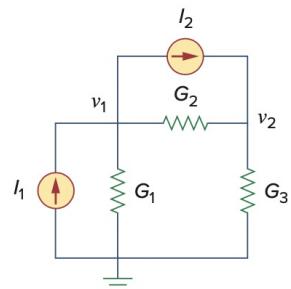

- When all elements are independent current sources, we don't need to apply KCL to each node. By inspection,

$$\begin{bmatrix} \Sigma G \text{ to node 1} \\ \Sigma G \text{ to node 2} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} \Sigma I @ 1 \\ \Sigma I @ 2 \end{bmatrix}$$

↓
Resultive of conductance
btw. nodes

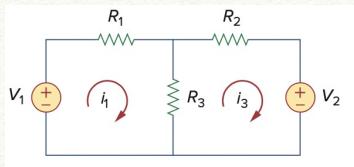

- If everything is voltage source,


$$\begin{bmatrix} ER \text{ in mesh 1} \\ R_1 + R_3 \\ -R_3 \\ R_2 + R_3 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} V_1 \\ -V_2 \end{bmatrix}$$

→ clockwise run first
clockwise

↳ ER in mesh 2

Invert sign of
resistors in middle.

Ex:

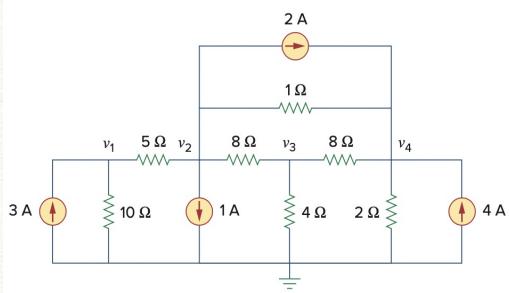

$$\begin{bmatrix} 0.3 & -\frac{1}{5} & 0 & 0 \\ -\frac{1}{5} & 1.325 & -\frac{1}{5} & -1 \\ 0 & -\frac{1}{8} & 0.5 & -\frac{1}{8} \\ 0 & -1 & -\frac{1}{4} & 1.625 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \end{bmatrix} = \begin{bmatrix} 3 \\ -3 \\ 0 \\ 6 \end{bmatrix}$$

$$V_1 = 13.90 \text{ V}$$

$$V_2 = 5.845 \text{ V}$$

$$V_3 = 3.398 \text{ V}$$

$$V_4 = 7.547 \text{ V}$$

$$G_{ii} = \frac{1}{10} + \frac{1}{5} = 0.3$$

$$G_{12} = G_{21} = -\frac{1}{5} = -0.2$$

$$G_{22} = \frac{1}{8} + \frac{1}{3} + \frac{1}{1} = 1.325$$

$$G_{33} = \frac{1}{8} + \frac{1}{8} + \frac{1}{4} = 0.5$$


$$G_{44} = \frac{1}{2} + \frac{1}{2} + \frac{1}{1} = 1.625$$

conductance must
✓ be direct (no resistor
in b/w)

- $G_{ii} \Rightarrow \Sigma$ conductance thru node i

- $G_{ij} \Rightarrow \Sigma$ conductance b/w node i and j

Cx_1

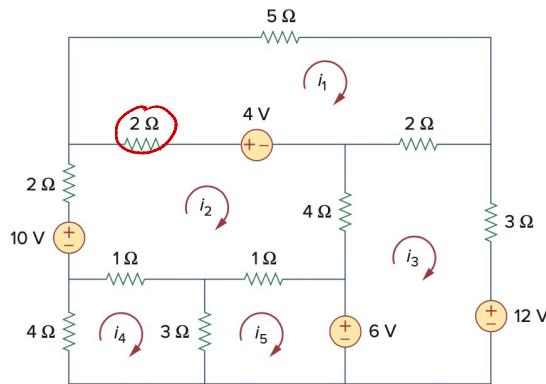

$$\begin{bmatrix} 9 & -2 & -2 & 0 & 0 \\ -2 & 10 & -4 & -1 & -1 \\ -2 & -4 & 9 & 0 & 0 \\ 0 & 1 & 0 & 8 & -3 \\ 0 & -1 & 0 & -3 & 4 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \end{bmatrix} = \begin{bmatrix} 4 \\ 6 \\ -6 \\ 0 \\ -6 \end{bmatrix}$$

- R_{ii} is Σ resistance in loop
- R_{ij} is $-\Sigma$ resistance in common w/ i and j .

NODAL VS. MESH ANALYSIS

Nodal Analysis	Mesh Analysis
↑ parallel elements	↑ series elements
↑ current sources	↑ voltage sources
↑ supernodes	↑ superloops
nodes < meshes	meshes < nodes
require node voltages	require currents