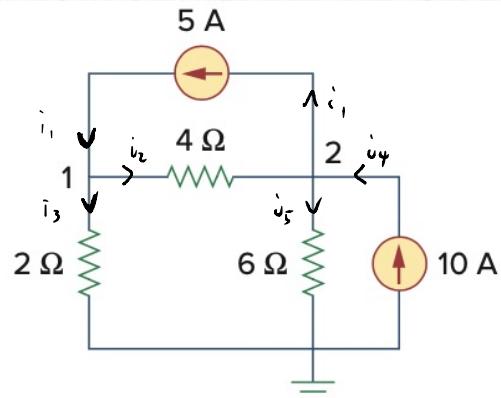


NODAL ANALYSIS

- We can express currents using Ohm's Law to simplify things
- uses KCL to find voltages

Ex: Calculate node voltages



(a)

$$\textcircled{1} \quad v_1 = i_2 + i_3$$

$$5 = \frac{v_1 - v_2}{4} + \frac{v_1 - 0}{2}$$

$$20 = v_1 - v_2 + 2v_1$$

$$20 = 3v_1 - v_2$$

$$\textcircled{2} \quad i_4 = i_1 + i_5$$

$$10 = 5 + \frac{v_2 - 0}{6}$$

$$60 = 30 + v_2$$


$$v_2 = 30 \text{ V}$$

$$\textcircled{2} \rightarrow \textcircled{1} \quad 20 = 3v_1 - 30$$

$$50 = 3v_1$$

$$v_1 = \frac{50}{3} = 16.7 \text{ V}$$

CY.

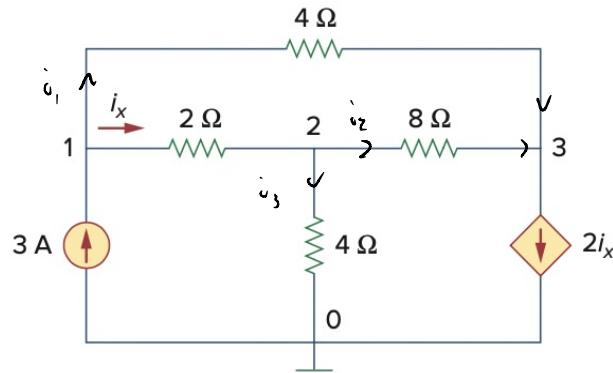

(a)

$$\textcircled{1} \quad 3 = i_1 + i_x$$

$$3 = \frac{V_1 - V_3}{4} + \frac{V_1 - V_2}{2}$$

$$\textcircled{2} \quad i_x = i_2 + i_3$$

$$\frac{V_1 - V_2}{2} = \frac{V_2 - V_3}{8} + \frac{V_2}{4}$$

$$\textcircled{3} \quad 2i_x = i_2 + i_1$$

$$2\left(\frac{V_1 - V_2}{2}\right) = \frac{V_2 - V_3}{8} + \frac{V_1 - V_3}{4}$$

$$12 = V_1 - V_3 + 2V_1 - 2V_2$$

$$4V_1 - 4V_2 = V_2 - V_3 + 2V_2$$

$$8V_1 - 8V_2 = V_2 - V_3 + 2V_1 - 2V_3$$

$$12 = 3V_1 - 2V_2 - V_3$$

$$4V_1 - 7V_2 + V_3 = 0$$

$$6V_1 - 9V_2 + 3V_3 = 0$$

$$2V_1 - 3V_2 + V_3 = 0$$

$$\textcircled{1} \quad 2V_1 - 3V_2 + V_3 = 0$$

$$\textcircled{2} \quad 4V_1 - 7V_2 + V_3 = 0$$

$$\textcircled{3} \quad 3V_1 - 2V_2 - V_3 = 12$$

$$V_3 = 3(2.4) - 2(4.8)$$

$$= -2.4 \text{ V}$$

$$\textcircled{1} + \textcircled{2} : 5V_1 - 5V_2 = 12$$

$$\textcircled{2} - \textcircled{1} : 2V_1 - 4V_2 = 0$$

$$V_1 - 2V_2 = 0$$

$$V_1 = 2V_2$$


$$10V_2 - 5V_2 = 12$$

$$V_2 = \frac{12}{5} = 2.4 \text{ V}$$

$$V_1 = 4.8 \text{ V}$$

$$V_3 = -2.4 \text{ V}$$

WITH VOLTAGE SOURCES

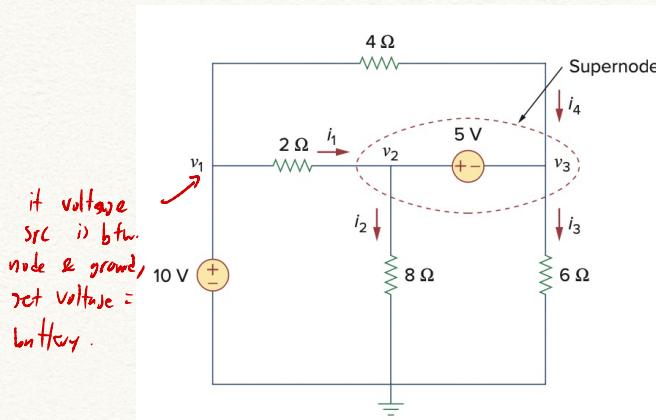

✓ if voltage src is b/w two non-ground nodes, can combine into supernode.


- KCL must still hold over a supernode. i.e. $i_1 + i_4 = i_2 + i_3$

$$\Rightarrow \frac{V_1 - V_2}{2} + \frac{V_1 - V_3}{4} = \frac{V_2}{8} + \frac{V_3}{6}$$

- at the supernode, $V_2 - V_3 = 5$ (KVL)

- ★ Voltage inside supernode provides an eqn. required to solve the system.
- ✗ Supernode has no voltage of its own
- ★ Supernode require application of KCL/KVL

Ex.

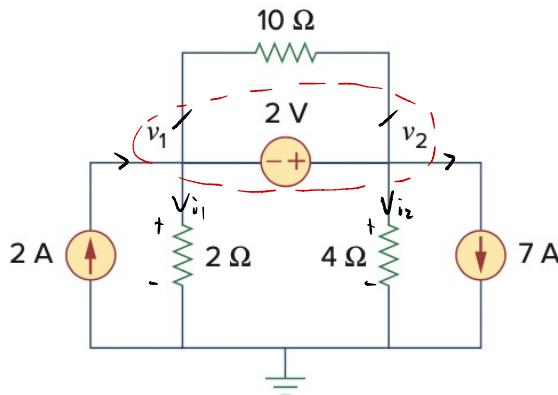

$$V_2 - V_1 = 2V$$

$$V_2 = 2 + V_1$$

KCL @ SN!

$$2 = i_1 + i_2 + 7$$


$$2 = \frac{V_1}{2} + \frac{V_1}{4} + 7$$

$$8 = 2V_1 + V_2 + 28$$

$$-20 = 2V_1 + 2 + V_1$$

$$-22 = 3V_1$$
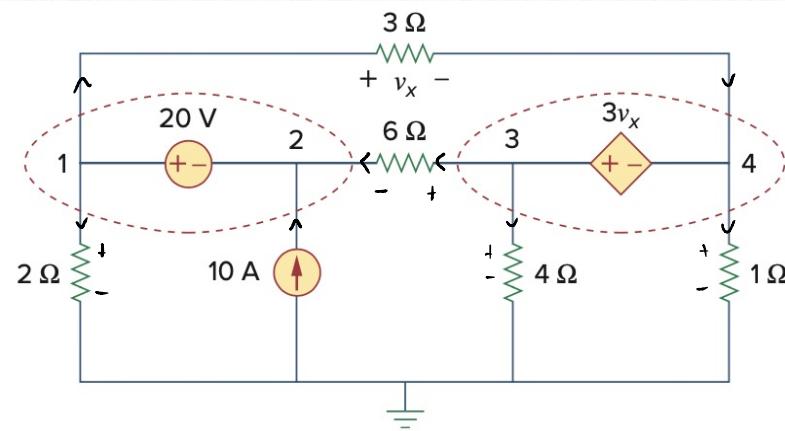
$$V_1 = -\frac{22}{3} V \quad V_2 = -\frac{16}{3}$$



$$V_1 - V_2 = 20$$

KCL @ SN1:

$$V_3 - V_4 = 3V_x$$

$$V_x = \frac{V_1 - V_4}{3}$$

$$V_3 - V_2 + 60 = 3V_1 + 2V_2 - 2V_4$$

$$V_3 - V_4 = 3V_1 - 3V_4$$

$$\Rightarrow 3V_1 - V_3 - 2V_4 = 0$$

$$\left\{ \begin{array}{l} 5V_1 + V_2 - V_3 - 2V_4 = 60 \\ 4V_1 + 2V_2 - 5V_3 - 16V_4 = 0 \\ 3V_1 - V_3 - 2V_4 = 0 \\ V_1 - V_2 = 20 \end{array} \right.$$

$$\frac{V_1 - V_4}{3} = \frac{V_4}{1} + \frac{V_2}{4} + \frac{V_3 - V_2}{6}$$

$$8V_1 - 8V_4 = 24V_4 + 6V_3 + 4V_2 - 4V_2$$

$$V_1 = \frac{80}{3} \quad V_2 = \frac{20}{3} \quad V_3 = \frac{520}{3} \quad V_4 = -\frac{140}{3}$$

$$V_1 = 26.7 \text{ V} \quad V_2 = 6.7 \text{ V} \quad V_3 = 173.3 \text{ V} \quad V_4 = -46.7 \text{ V}$$