

# LINEAR CIRCUITS

Linearity is property describing linear relation b/w cause/effect

- has to satisfy proportionality & additivity

- proportionality (homogeneity)

$$\rightarrow V = iR$$

$$\Rightarrow KiR = KV$$

- additivity

$$\rightarrow V_1 = i_1 R, V_2 = i_2 R$$

applying  $i_1 + i_2$  gives

$$V = (i_1 + i_2)R = i_1 R + i_2 R = V_1 + V_2$$

- $P = i^2 R \rightarrow$  non linear but quadratic

## SUPERPOSITION

if circuit has  $z^+$  independent sources, can

1. use nodal/mesh analysis

2. use superposition


→ determine contribution of each source and add.

### method

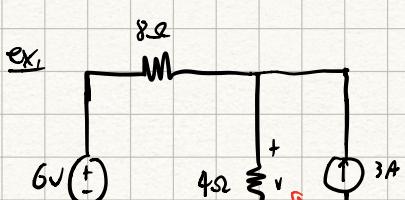1. turn off all independent sources but one. Find voltage/current due to that source
2. repeat for other sources
3. add them up.

\* Current sources become open; voltage sources are shorted.

- usually takes lots of work; 3 sources = 3 circuits




contribution by 6V

1. turn on 6V



Let  $V = V_1 + V_2$  ← continuation of


To find  $V_1$ , set  $V_2 = 0$

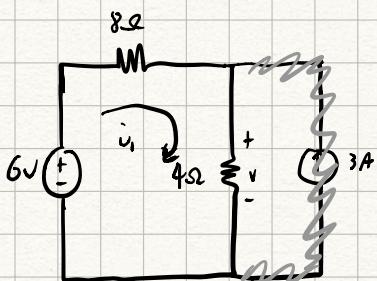

KVL:

$$6 = (8+4)i_1 \\ i_1 = \frac{1}{2} A \\ V_1 = 4(i_1) = 2V$$

To find  $V_2$ , set  $V_1 = 0$

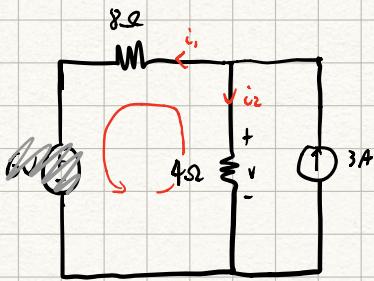

KCL:  
 $3 = i_1 + i_2$

KVL:  
 $9i_1 = 4i_2 \\ i_2 = 2i_1$

We can also use voltage division:

$$V_1 = \frac{4}{4+8}(6) = 2V$$

We can use current division:

$$i_2 = \frac{8}{8+4}(3) = 2A$$


$$\Rightarrow i_1 = 1A \\ i_2 = 2A \\ V_2 = 2(4) = 8V$$

$$V = V_1 + V_2 = 2 + 8 = 10V$$

Q15v...  $i_{42} = \frac{1}{2} + 2 = 2.5A$  down

$i_{23} = \frac{1}{2} - 1 = 0.5A$  left

Ex1

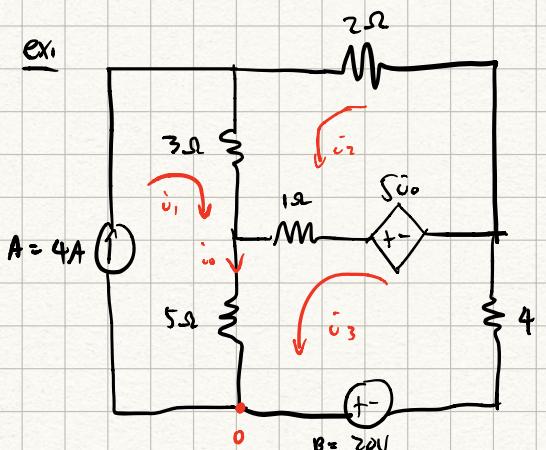

Find  $v_o$  using superposition

$$i_o = i_{oA} + i_{oB}$$

turn off 20V!

Loop 1:	$i_1 = 4A$
Loop 2:	$3i_1 + 6i_2 - i_3 + 5i_{oA} = 0$
Loop 3:	$-5i_{oA} + 5i_1 - i_2 + 10i_3 = 0$
Node 0:	$i_o = i_1 + i_3$
	$i_o - i_1 - i_3 = 0$


$$i_{oA} = \frac{5^2}{17} A$$


turn off 4A!

Loop 4:	$5i_{oB} + 6i_4 + i_5 = 0$
Loop 5:	$5i_{oB} + i_4 + 10i_5 = 20$
Node 1:	$i_{oB} + i_5 = 0$

$$i_{oB} = -\frac{60}{17}$$

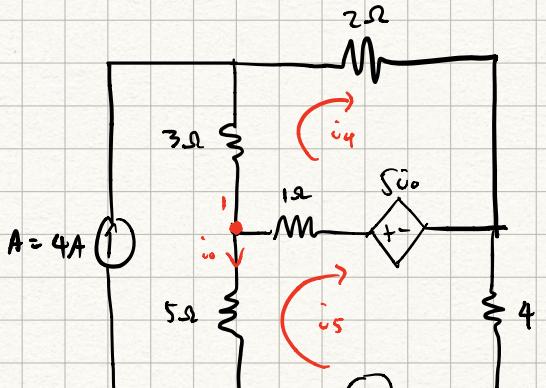
$$i_o = i_{oA} + i_{oB} = \frac{5^2}{17} - \frac{60}{17} = -\frac{8}{17} A$$



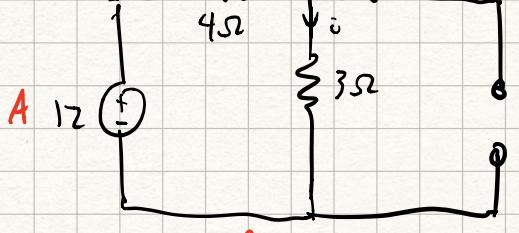

$$\frac{1}{12} + \frac{1}{4} = 3\Omega + 3\Omega = 6\Omega$$

$$i_4 = \frac{12}{6} = 2A$$

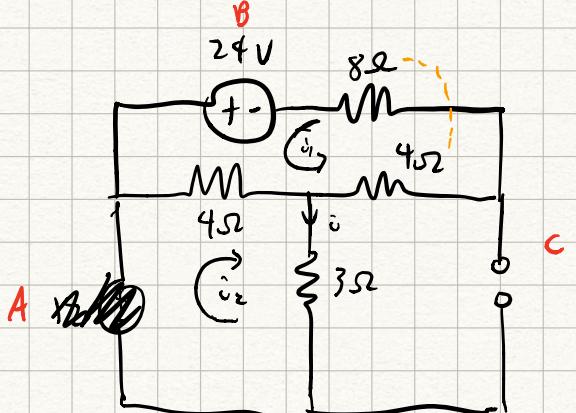


**B'**

$$\begin{aligned} 24 &= 16 i_1 + 4 i_2 \\ 6 &= 4 i_1 + i_2 \\ 0 &= 4 i_1 + 7 i_2 \end{aligned}$$

$$\begin{aligned} i_1 &= \frac{7}{4} \\ i_2 &= -1 \end{aligned}$$

**C'**

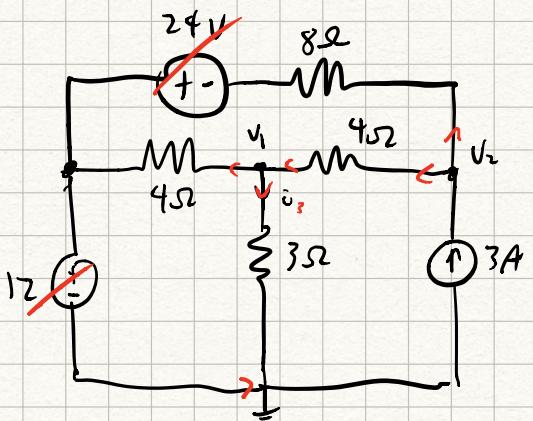

$$@ V_2 : \quad 3 = \frac{V_2}{8} + \frac{V_2 - V_1}{4}$$

$$\Rightarrow 24 = -2V_1 + 3V_2$$

$$@ V_1 : \quad \frac{V_1}{3} + \frac{V_1}{4} = \frac{V_2 - V_1}{9}$$

$$\Rightarrow 7V_1 = 3V_2 - 3V_1$$

$$\Rightarrow 10V_1 = 3V_2$$

$$\Rightarrow 10V_1 - 3V_2 = 0$$

$$V_1 = 3$$

$$V_2 = 10$$

$$i_3 = \frac{V_1}{3} = 1A$$

$$\text{So } i = 2 - 1 + 1 = 2A.$$