

OPERATIONAL AMPLIFIERS

Mar. 3, 2020





→ amplifying signal

→ building block of analog circuitry

→ behaves like voltage-controlled voltage source

→ designed to perform mathematical operations like

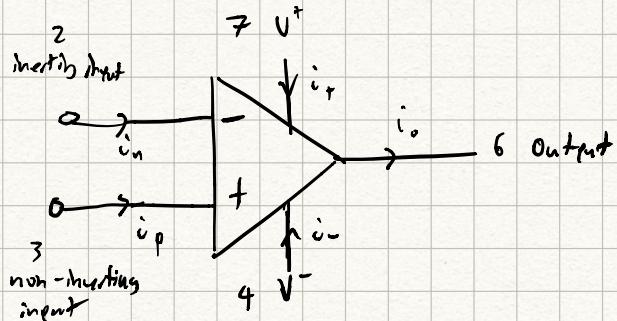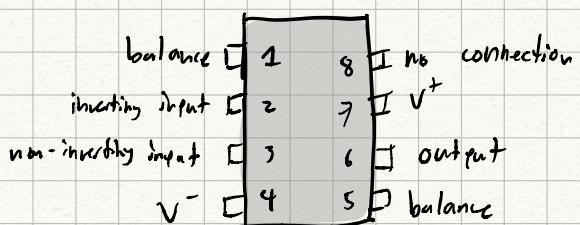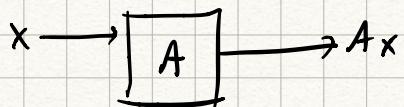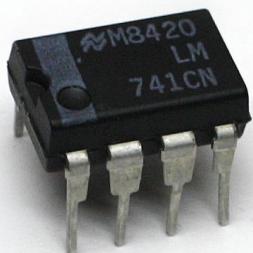- addition
- subtraction
- multiplication
- division
- differentiation
- integration




has differential input


$$\rightarrow V_o = A(V_p - V_n)$$

A is known as gain, is a scaling factor

→ usually between $10^5 - 10^6$

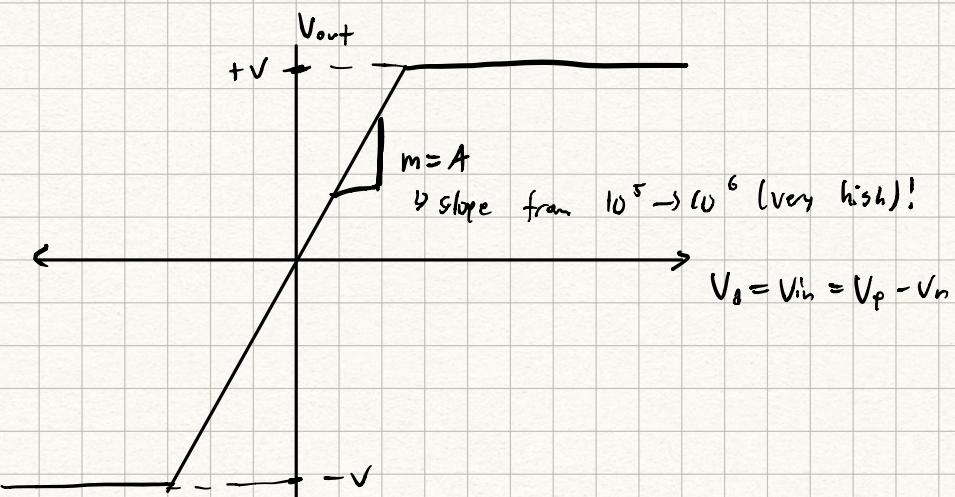

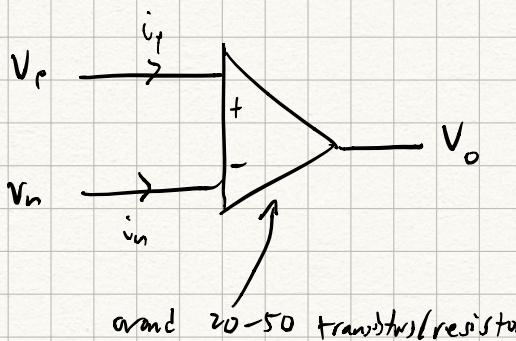→ cannot exceed power supply!
→ known as saturation





ideally!

$$i_1 = i_2 = 0$$

$$V_o = A(V_p - V_n)$$


$$V_o = A V_{in}$$

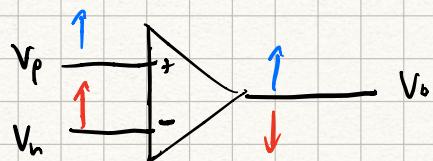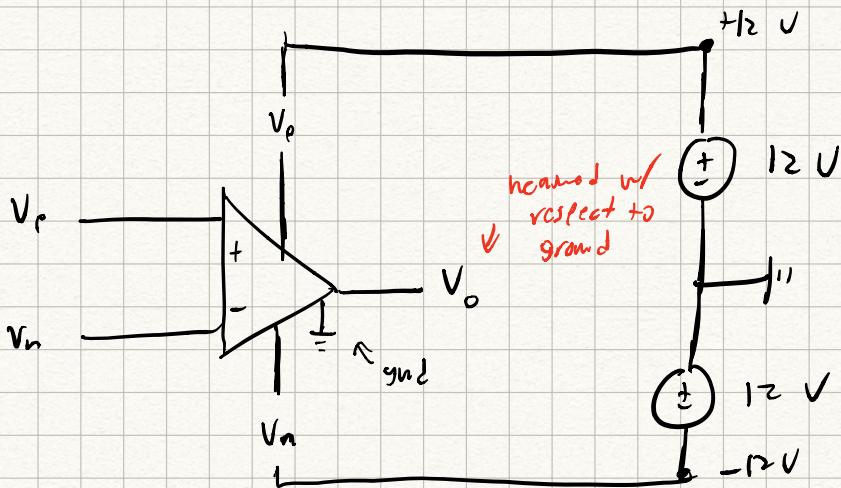

Since $V_o = A(V_p - V_n)$, when

$V_p \uparrow$, $V_o \uparrow$. Thus V_p is **non-inverting input**

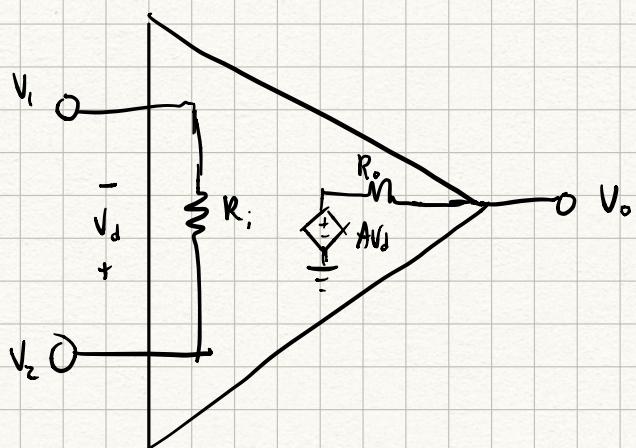$V_n \uparrow$, $V_o \downarrow$. Thus V_n is **inverting input**



R_i is **Thevenin equivalent resistance b/w input terminals**

R_o is **output resistance, or Thevenin equivalent resistance at output**

★ in an **ideal** op-amp, $R_{out} = 0$.

$$\hookrightarrow V_o = A(V_p - V_n)$$

★ we assume op-amp operates in **linear range**



★ R_{in} is usually **really high**
→ why?

non-ideal op-amp

Ex.

741 op-amp has open loop voltage gain of 2×10^5
input resistance of $2 M\Omega$
output resistance of 50Ω .

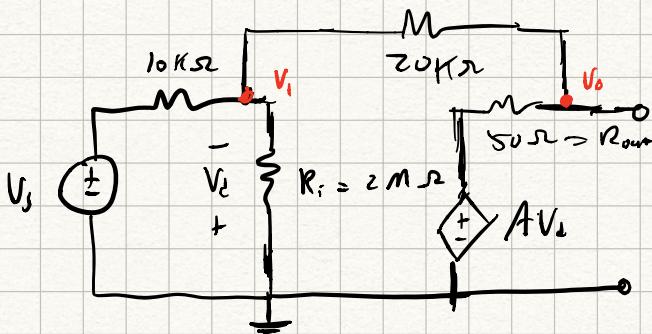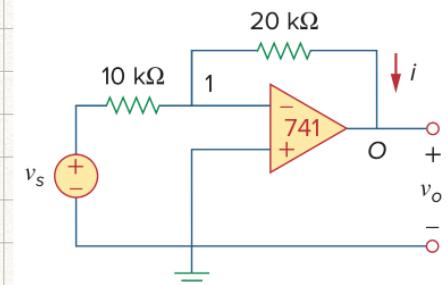Find closed loop gain $\frac{V_o}{V_s}$. Find i when $V_s = 2V_i$.



at node 1:

$$\frac{V_s - V_1}{10 \times 10^3} = \frac{V_1}{2 \times 10^6} + \frac{V_1 - V_o}{20 \times 10^3}$$

$$V_1: 200(V_s - V_1) = V_1 + 100(V_1 - V_o)$$

$$200V_s = 301V_1 - 100V_o$$

$$2V_s \approx 3V_1 - V_o \Rightarrow V_1 = \frac{2V_s + V_o}{3}$$

$$V_o: \frac{V_o - AV_1}{50} = \frac{V_1 - V_o}{20 \times 10^3}$$

$$V_o = -V_1, A = 2 \times 10^5$$

$$\Rightarrow \frac{V_o + (2 \times 10^5)(V_1)}{50} \approx \frac{V_1 - V_o}{20 \times 10^3}$$

$$400V_o + 8 \times 10^7 V_1 = V_1 - V_o$$

$$400V_o + 8 \times 10^7 \left(\frac{2V_s + V_o}{3} \right) = \left[\frac{2V_s + V_o}{3} \right] - V_o$$

$$0 \approx 26,667,067V_o + 53,333,333V_s$$

$$\frac{V_o}{V_s} = -1.9999699$$

→ closed loop gain, since $20\text{ k}\Omega$ connects input & output

When $V_s = 2$, $V_o = -3,9999318 \text{ V}$.

$$V_o = \frac{2(z) - 3,9999318}{z} = 20.06667 \text{ mV.}$$

$$i = \frac{V_i - V_o}{20 \times 10^3} = 0.199999 \text{ mA.}$$


→ dealing w/ non-ideal op-amps are tedious since numbers are really large & need to be precise.

IDEAL OP-AMP


Mar. 02, 2020

* ideal op-amps are...

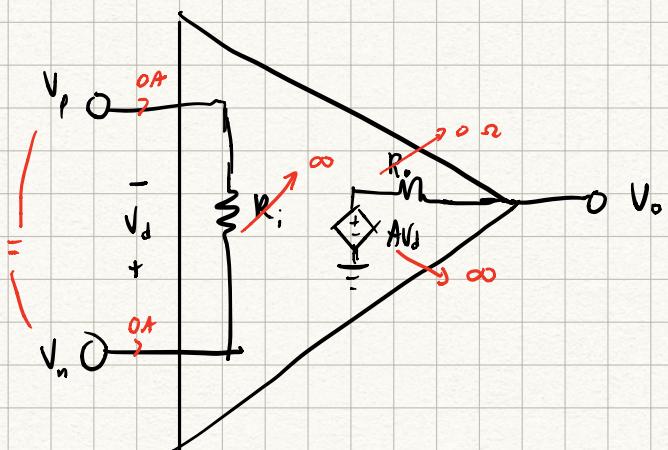
1. ∞ open loop gain, $A \approx \infty$
2. ∞ input resistance, $R_i \approx \infty$
3. 0 output resistance, $R_o \approx 0$



ideal op amp

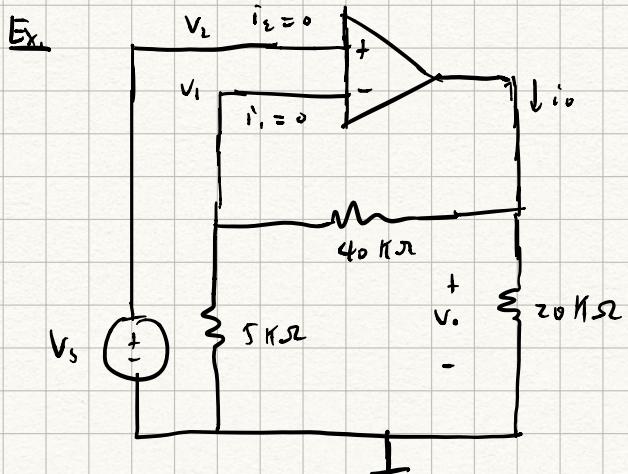

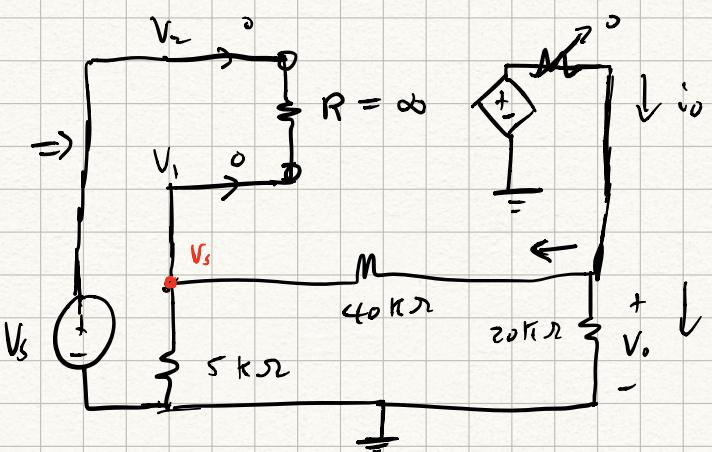Calculate $\frac{V_o}{V_s}$ and i_o when $V_s = 1 \text{ V}$.



$$V = V_i = V$$

$$R_{eq} = (40 + 5)$$

$$V_1 = \frac{5}{5+40} V_o = \frac{V_o}{9}$$

$$V_2 - V_1 = V_s \text{ and } V_2 = V_1, \text{ so } V_1 = V_s.$$

$$\therefore V_s = \frac{V_o}{9}$$

$$\therefore \frac{V_o}{V_s} = 9$$

$$\text{When } V_s = 1, V_o = 9$$

$$\Rightarrow V_1 = \frac{1}{9}$$


$$i_o = \frac{V_o}{20 \times 10^3} + \frac{V_o - V_s}{40 \times 10^3}$$

$$i_o = \frac{9}{20 \times 10^3} + \frac{9}{45 \times 10^3}$$

$$i_o = 0.65 \text{ mA}$$

INVERTING AMPLIFIER

→ We want to invert an input voltage.

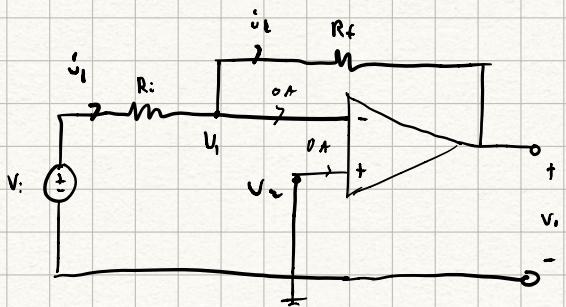


$$i_1 = i_2 = \frac{V_i - V_o}{R_i + R_f} \rightarrow \text{this isn't helpful b.c. we want relationship btw. } V_i \text{ & } V_o.$$

$$\Rightarrow \frac{V_i - V_o}{R_i} = \frac{V_o}{R_f}$$

Since $V_1 = V_2 = 0$ (ideal op amp),

$$V_i = -\frac{R_f}{R_i} V_o$$

NON-INVERTING AMPLIFIER

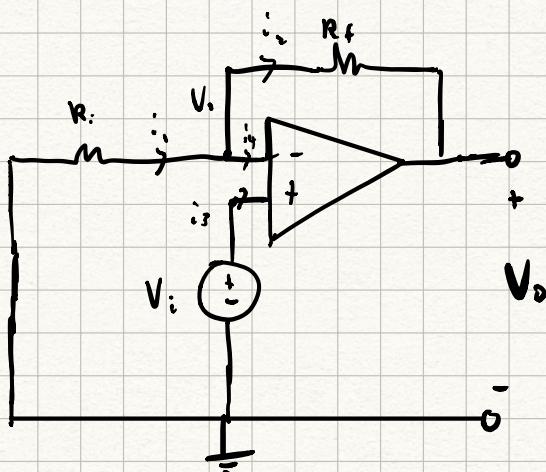

$$i_1 = i_2 = 0$$

$$v_1 = v_2 = \frac{V_i - V_o}{R_f} = \frac{V_o - V_i}{R_f}$$

$$V_i = V_1$$

$$\Rightarrow \frac{V_i - V_o}{R_f} = \frac{-V_i}{R_i}$$

$$V_o = \left(1 + \frac{R_f}{R_i}\right) V_i$$


$$\frac{V_i}{R_i} + \frac{V_i}{R_f} = \frac{V_o}{R_f}$$

$$V_i R_f \left(\frac{1}{R_i} + \frac{1}{R_f}\right) = V_o$$

if $R_i = \infty$ (O.C), $V_o = V_i$


if $R_f = 0$ (S.C), $V_o = V_i$

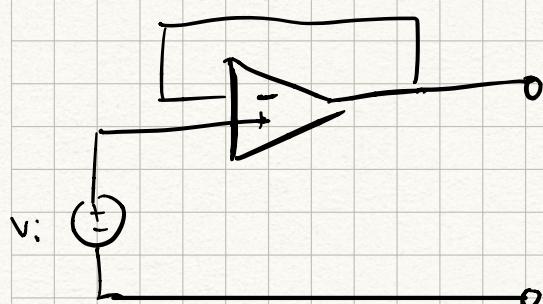When $V_o = V_i$, we call it a **voltage follower** or **unity gain amplifier**




Voltage follower

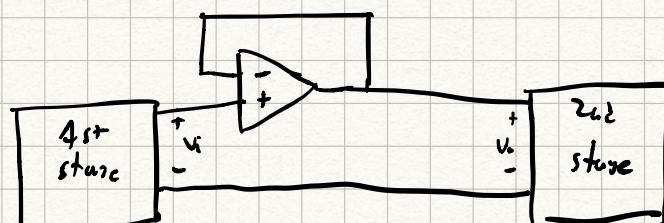→ used to isolate two stages of cascading circuit.



SUMMING AMP.

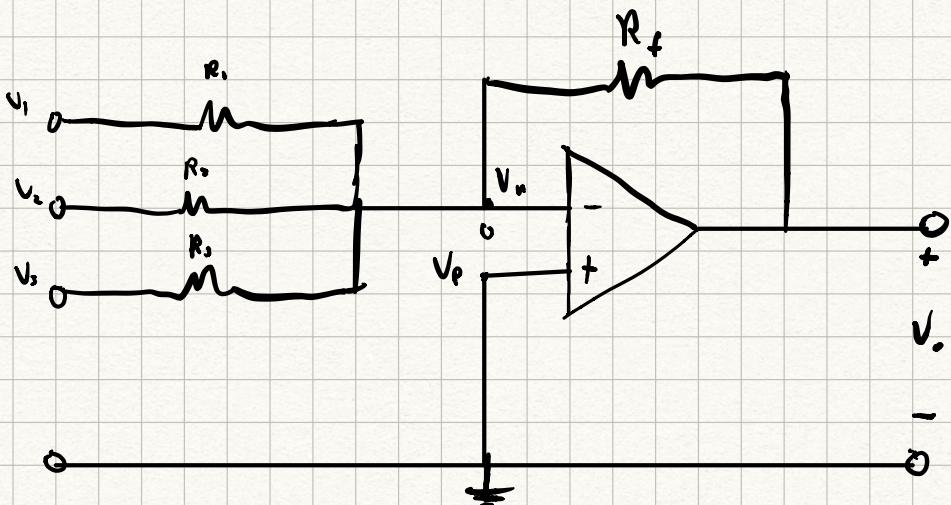→ takes multiple inputs and produces output that is weighted sum of inputs




$$V_n = V_o = 0$$

$$\frac{V_1 - V_n}{R_1} + \frac{V_2 - V_n}{R_2} + \frac{V_3 - V_n}{R_3} = \frac{V_n - V_o}{R_f}$$

$$V_o = -R_f \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right)$$

DIFF. AMP.

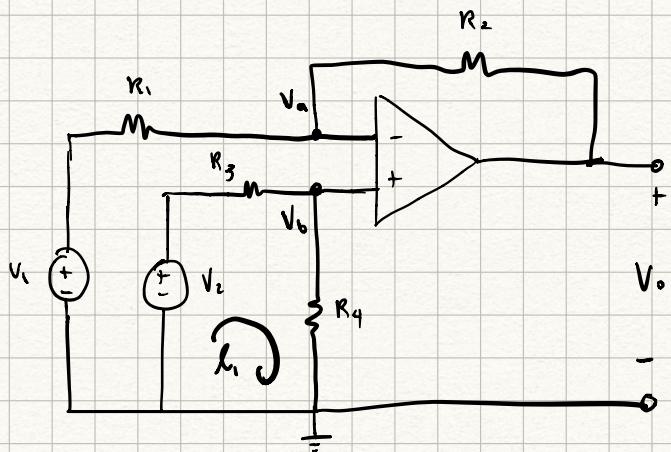

$$\frac{V_1}{R_1} = \frac{V_a - V_b}{R_2}$$

KVL Rule:

$$V_2 = i(R_3 + R_4)$$

$$V_2 = \frac{R_4}{R_3 + R_4} V_o$$


$$V_b = V_a$$

$$\Rightarrow \frac{V_1}{R_1} = \frac{\frac{R_4}{R_3 + R_4} V_2 - V_b}{R_2}$$

$$\frac{R_2}{R_1} V_1 = \frac{R_4}{R_3 + R_4} V_2 - V_b$$

$$V_o = \frac{R_4}{R_3 + R_4} V_2 - \frac{R_2}{R_1} V_1$$

ADDER AMPLIFIER

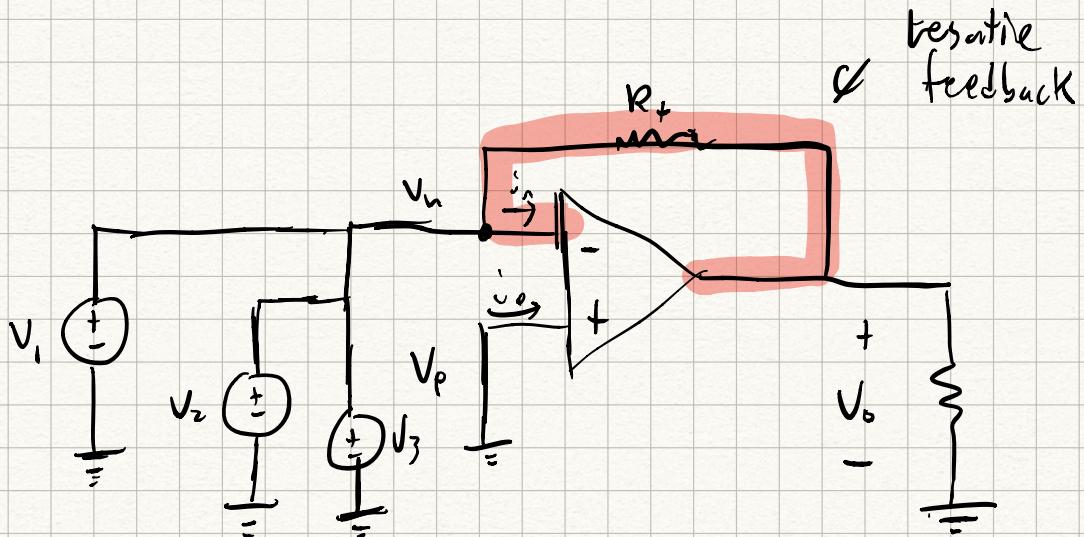

KCL at V_b


$$\frac{V_n - V_1}{R_1} + \frac{V_n - V_2}{R_2} + \frac{V_n - V_3}{R_3} + \frac{V_n - V_o}{R_f} = 0$$

$$V_o = - \left(\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 \right)$$

→ Swapping (+) and (-) has no effect

→ becomes positive feedback / driving into saturation


→ negative feedback always

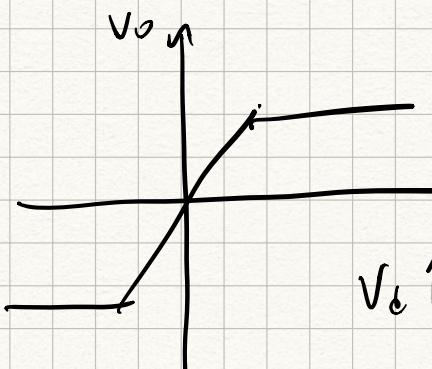

$V_o \uparrow$ when positive feedback Loop

→ V_o initially large, neg. feedback takes int. linear region

DIFFERENCE AMPLIFIER

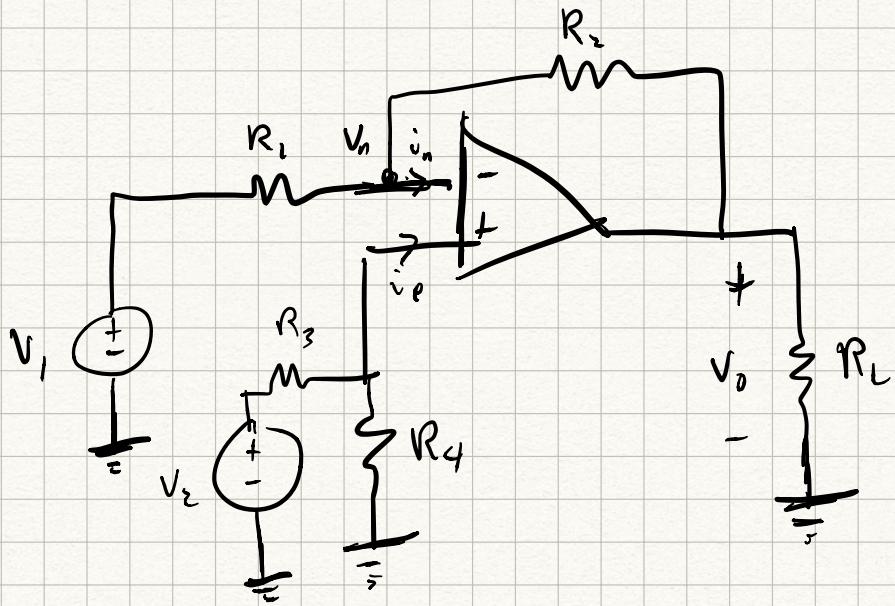

KCL @ V_n:

$$\frac{V_n}{R_1} - \frac{V_1}{R_1} + \frac{V_n}{R_2} - \frac{V_2}{R_2} = 0$$

$$\frac{V_n - V_1}{R_1} + \frac{V_n - V_2}{R_2} + i_n^0 = 0$$


$$V_n = \left(\frac{R_2}{R_1} + 1 \right) V_2 - \left(\frac{R_2}{R_1} \right) V_1$$

$$\begin{aligned} V_p = V_n &= \frac{R_4}{R_3 + R_4} \cdot V_2 \\ &= \frac{1}{\left(\frac{R_3}{R_4} + 1 \right)} \cdot V_2 \end{aligned}$$

$$V_o = \frac{\left(\frac{R_2}{R_1} + 1 \right)}{\left(\frac{R_3}{R_4} + 1 \right)} V_2 - \left(\frac{R_2}{R_1} \right) V_1$$

$$= \frac{R_2}{R_1} \left[\frac{\frac{R_1}{R_2} + 1}{\frac{R_3}{R_4} + 1} V_2 - V_1 \right]$$
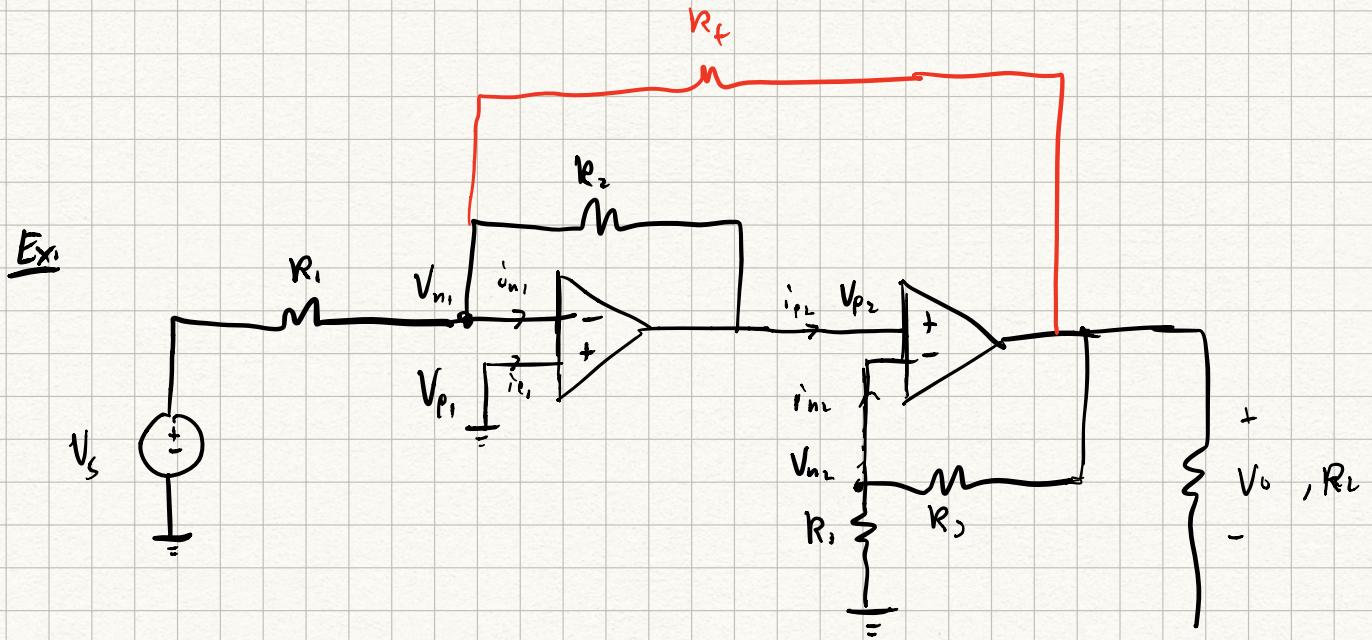
$$\text{At } V_{in} \quad \frac{R_1}{R_2} = \frac{R_3}{R_4} \Rightarrow V_o = \frac{R_3}{R_1} (V_2 - V_1)$$



$$V_{p1} = 0$$

$$V_{n1} = 0$$

KCL @ V_{n1}

$$\frac{V_{n1} - V_s}{R_1} + \frac{V_{n1} - V_{p2}}{R_2} + i_{n1} = 0$$

$$V_s = -\frac{R_1}{R_2} V_{p2} \quad \text{or} \quad \boxed{V_{p2} = -\frac{R_2}{R_1} V_s}$$

$$V_{n2} = V_{p2}$$

KCL @ V_{n2}

$$\frac{V_{n2}}{R_4} + \frac{V_{n2} - V_o}{R_3} + i_{n2} = 0$$

$$= -\frac{R_2}{R_1 R_4} V_s - \frac{R_2}{R_1 R_3} V_s - \frac{V_o}{R_3} = 0$$

$$V_o = -\left(\frac{R_2}{R_1}\right) \left(1 + \frac{R_3}{R_4}\right) V_s$$

$$R_1 = R_4 = 2k\Omega$$

$$R_2 = R_3 =$$

$$G_v = \frac{V_o}{V_i} = - \underbrace{\left(1 + \frac{Z_o}{Z_s}\right)}_{11} \underbrace{\left(\frac{Z_o}{Z_s}\right)}_{10}$$

$$G_v = -110 \text{ V.}$$