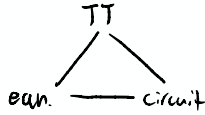


TRUTH TABLES

- one way to express a logic function



can convert b/w. all 3.

- there will be 2^n combinations, where n is the # inputs

x_0	x_1	x_2	f
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

EQUATION FORM

$$f = \bar{x}_2 \bar{x}_1 \bar{x}_0 + \bar{x}_2 x_1 x_0 + x_2 x_1 x_0$$

rows with 1s: **minterms**

rows with 0s: **maxterms**

LOGICAL OPERATORS

- 3 basic logical operators: **AND, OR, NOT**

- **AND**: denoted by \cdot or $"$

ex. $f = x_1 \cdot x_0 = x_1 x_2$



x_0	x_1	$f = x_1 x_0$
0	0	0
0	1	0
1	0	0
1	1	1

\Rightarrow

x_0	x_1	...	x_{n-2}	x_{n-1}	$f = x_{n-1} x_{n-2} \dots x_1 x_0$
0	0	...	0	0	0
0	0	...	0	1	0
...
0	1	...	1	1	0
1	0	...	0	0	0
1	0	...	0	1	0
...
1	1	...	1	1	1

- OR: denoted by $+$
ex. $f = x_1 + x_0$




x_0	x_1	$f = x_1 x_0$
0	0	0
0	1	1
1	0	1
1	1	1

\Rightarrow

x_0	x_1	...	x_{n-2}	x_{n-1}	$f = x_{n-1} x_{n-2} \dots x_1 x_0$
0	0	...	0	0	0
0	0	...	0	1	1
...
0	1	...	1	1	1
1	0	...	0	0	1
1	0	...	0	1	1
...
1	1	...	1	1	1

- NOT: denoted by $!$, $'$, \neg , $\bar{}$
ex. $f = !x = x' = \neg x = \bar{x}$

x	$f = !x$
0	1
1	0

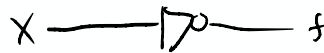


"0" inverts something is being inverted
"1" buffer (amplifies signal aka voltage repeater)

x	f
0	1
1	0

- XOR: denoted by \oplus


a	b	y
0	0	0
0	1	1
1	0	1
1	1	0

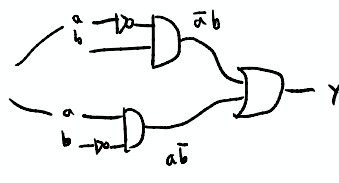


$$f = \bar{a}b + a\bar{b} = a \oplus b$$




CIRCUIT DIAGRAM

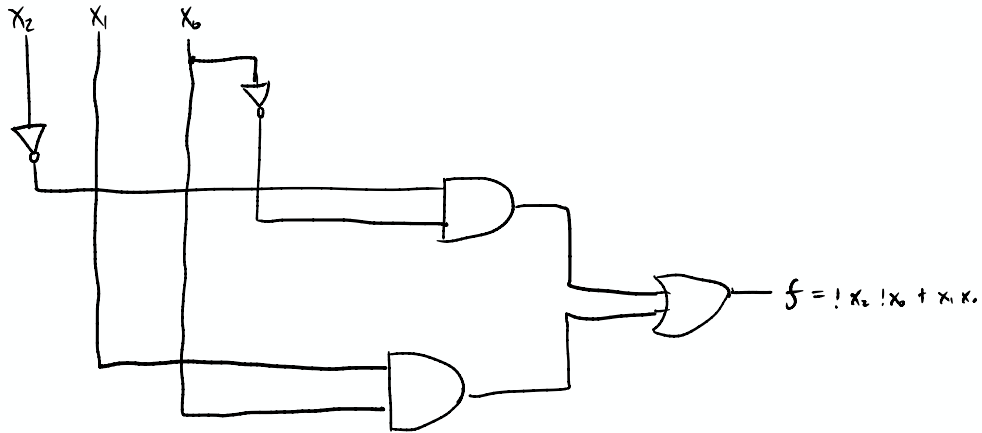


SUM OF PRODUCTS

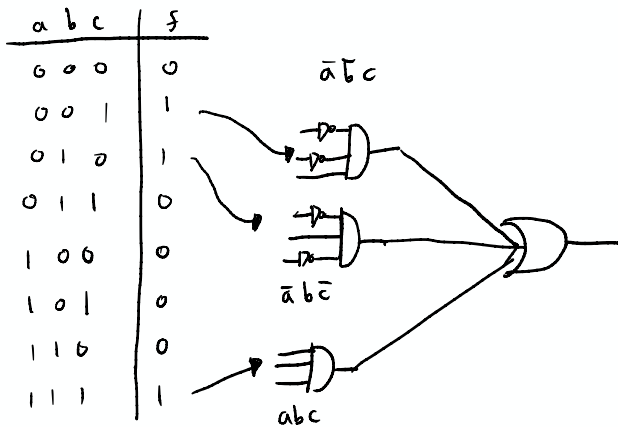


PRODUCT OF SUM

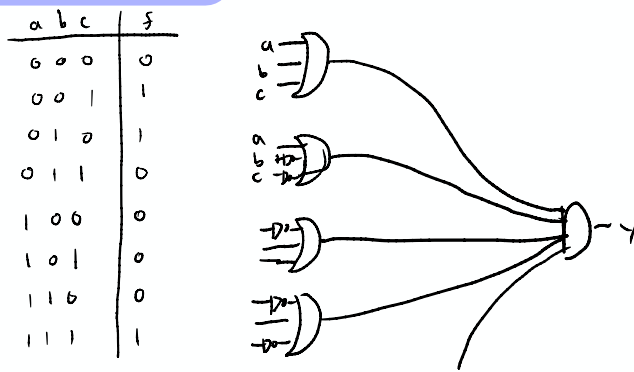

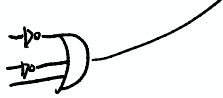


a	b	y	q
0	0	1	0
0	1	0	1
1	0	1	0
1	1	1	0


P.O.S

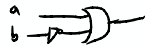

S.O.P

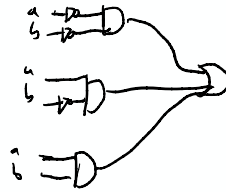

S.O.P'

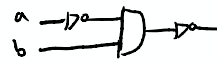

$$xy + \bar{x}z + yz = xy + \bar{x}z$$

Hi!

$$\begin{aligned}
 & xy + \bar{x}z + yz \cdot 1 \\
 &= xy + \bar{x}z + yz(x + \bar{x}) \\
 &= xy + \bar{x}z + xyz + \bar{x}yz \\
 &= xy(1 + z) + \bar{x}z(1 + z) \\
 &= xy + \bar{x}z
 \end{aligned}$$

GATES

$$\Rightarrow \text{AND gate with NOT on output} = \text{NAND gate}$$

$$\Rightarrow \text{OR gate with NOT on output} = \text{NOR gate}$$

$$\Rightarrow \text{AND gate with NOT on both inputs and output} = \text{NOR gate}$$

UNARY FUNCTION



$$\begin{aligned}
 y &= \text{NAND}(a, b) = \overline{ab} \\
 \text{NAND}(a, a) &= \overline{aa} = \bar{a}
 \end{aligned}$$