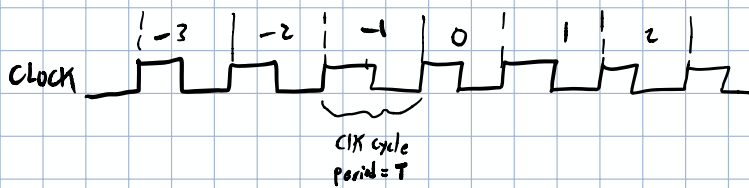


# SEQUENTIAL SYSTEM

So far, we've looked @ **pure functions**  
→ takes in input, outputs #

Soe time, we need to remember what happens  
→ state

- all sequential systems will have CLK signal
- all subsystems run off the clock



- has index, which is relative
- on schematic, clock looks like



+ positive edge  
- negative edge

- to insert function, insert clock





discrete time  
→ no units
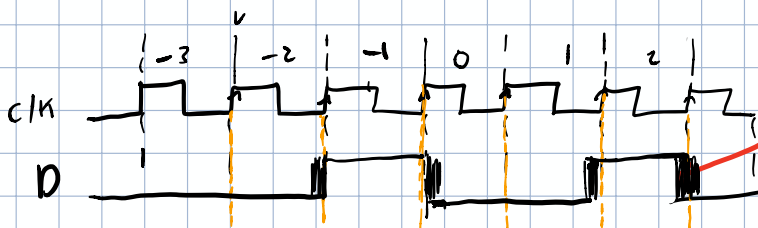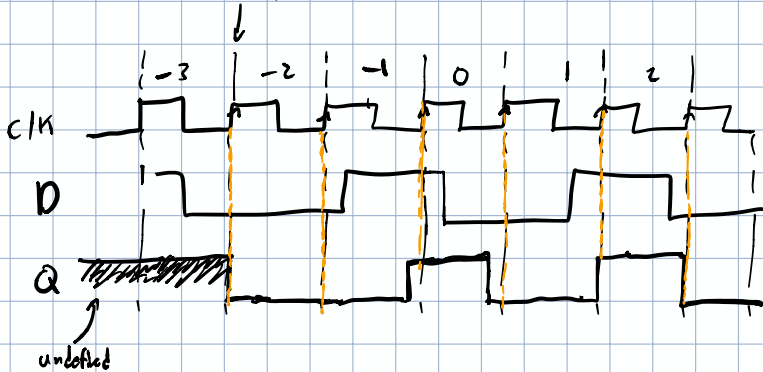
## DELAY



Delay propagates input → output on positive edge of clock  
first iter.






A sequential circuit...


- 1) receive binary information from external inputs
- 2) use these inputs along w/ present state to determine binary values of output
- 3) external inputs determine conditions for changing state in storage elements.

Always in this format!

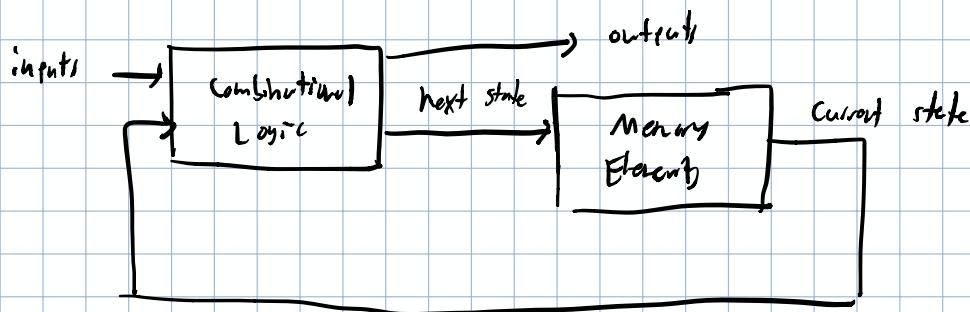

**synchronous sequential circuit**: behavior can be determined by knowledge of signals at moment in time.

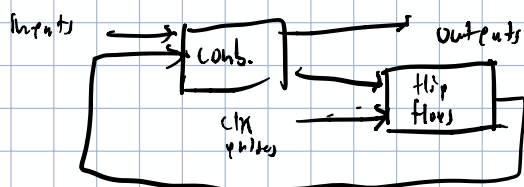- ↳ use flip-flops, which store 1 bit of information
- ↳ to store  $x$  bits, use  $x$  flip flops



- outputs based by combinational logic, prev. state of flip flops, or both
- clk pulses need to be less than propagation delay!!

**asynchronous sequential circuit**: depends on input signals at any instant in time AND order in which inputs change

- ↳ storage elements are time-delay devices
- ↳ logic gates have significant propagation delay to provide storage
- ↳ combinational circuit w/ feedback