

# FLIP-FLOPS


- D latch with pulse in  $En$  is essentially flip-flop.
- as long as pulse remains at 1, changes in data input will change output  
↳ this is a problem! how to get rid of noise?

Q use the edge of a clock pulse instead of the active high

- Flip-flops solve this problem by either
  - 1) Configuring master/slave latch to prevent changes
  - 2) Produce flip-flop that triggers only during signal transition
 
## EDGE-TRIGGERED D FLIP-FLOP

→ Recall that latches save state & turning "s" on/off has no effect.



On positive edge, D is sampled and the state is "saved" in Y.


On negative edge, Y propagates to Q.

\* What if D changes multiple times through logic-1 state?  
↳ last value before negative edge is preserved.


Q how do we make it trigger on positive edge instead?  
↳ add another inverter

Alternatively,


$x$	$y$	AND	NAND
0	0	0	1
0	1	0	1
1	0	0	0
1	1	1	0

 

 - when  $CLK = 0$ ,  $S$  &  $R$  are active and state is stored
- when  $CLK = 1$ :
  - if  $D = 0, R = 0$ 
    - ↳ changing output has no effect while  $CLK = 1$
  - if  $D = 1, S = 0$ 
    - ↳ changing output has no effect while  $CLK = 1$



positive edge

 

negative edge

Similar to latch, but ">" indicates dynamic input, triggered at edge of CLK.

- edge-triggered D flip-flops are most efficient (least # of gates)

$D$	$Q(t+1)$
0	0
1	1


Characteristic table for DFF

# JK-FLIPFLOPS

3 operations can be performed with flip-flops;

 - 1) set to 1
- 2) reset to 0
- 3) complement output

The JK flip-flop can perform all of these three operations




- Has feedback as an extra layer of safety
  - ↳ set to 1 if previously zero & value is 1 & clk
  - ↳ also logic for inverting / hold.

$$D = JQ' + KQ$$

- J input sets Q to 1
- K resets Q to 0.

↳ when  $K=1$ ,  $D=0$  so  $Q=0$  when clk.

 - when  $J=K=1$ ,  $D=Q'$ , so Q is inverted.
- when  $J=K=0$ ,  $D=Q$ , so Q is held.




J	K	Q(t+1)
0	0	Q(t)
0	1	0
1	0	1
1	1	Q'(t)

# T FLIP-FLOP
 
## Toggle Flip-Flop

We can obtain a T flip flop by tying J & K together...



- J & K are always the same

→ if  $J=K=1$ , state toggle

→ if  $J=K=0$ , hold

- $D = JQ' + K'Q = TQ' + T'Q = T \oplus Q$   
     $J=K=T$  ↗

- useful for designing binary counters

T	$Q(t+1)$
0	$Q(t)$
1	$Q'(t)$

1, 1, 2, 3, 5, 8, 13