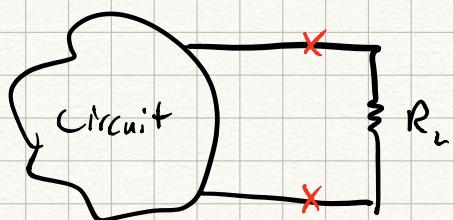




SOURCE TRANSFORMATION



How to find voltage across R_L ?


THEVENIN

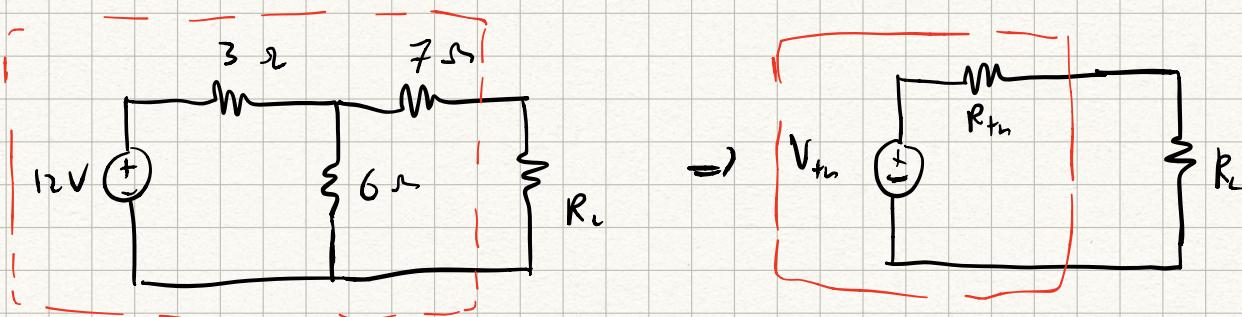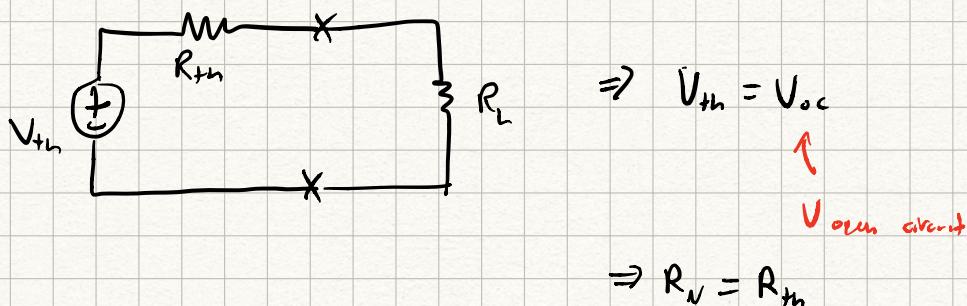- we can cut at Xs & replace entire circuit w/




$$V_{th} = V_{oc}$$

How to find V_{oc} ?

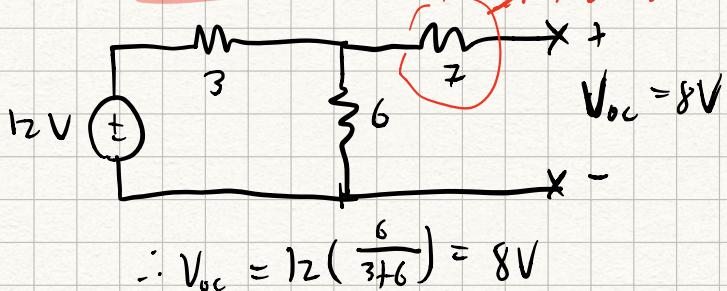


How to find R_{th} ?

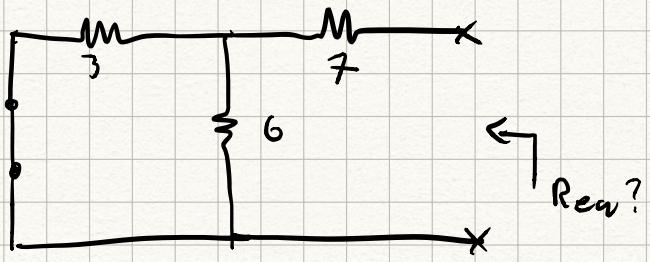⇒ if circuit has only independent sources, kill all sources and find R_{eq}




$$\begin{aligned}
 R_{eq} &= (3/6) + 7 \\
 &= \left(\frac{6 \cdot 3}{6+3}\right) + 7 \\
 &= 9 \Omega
 \end{aligned}$$

thus, the equivalent circuit is...

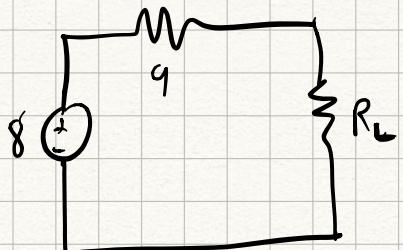


NORTON


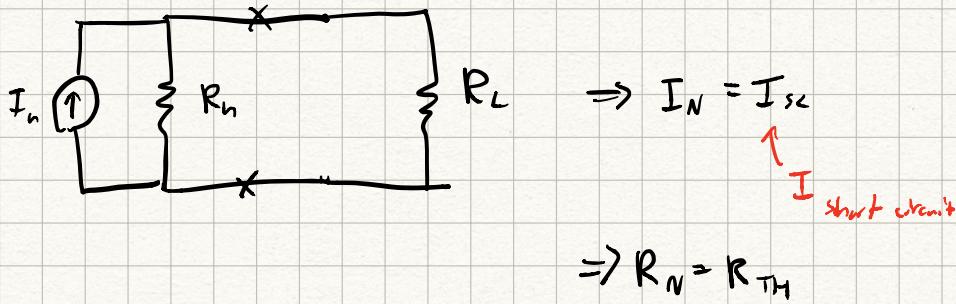


$$\Rightarrow R_N = R_{TH}$$


how to find I_N ?

$$I_N = I_{\text{short circuit.}}$$

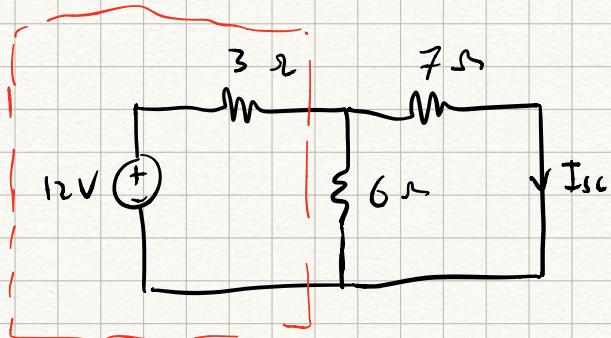


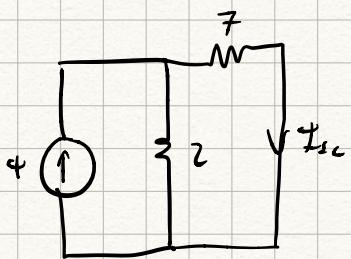
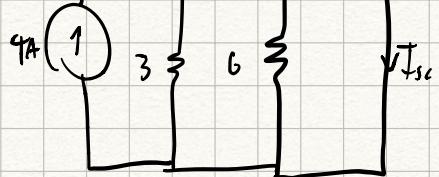

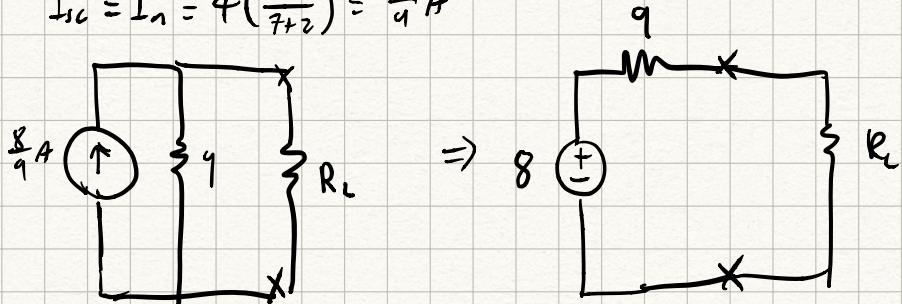
$$I_{th} = I_n = 9 \left(\frac{2}{7+2} \right) = \frac{8}{9} A$$



We can convert easiest b/w Thevenin & Norton!

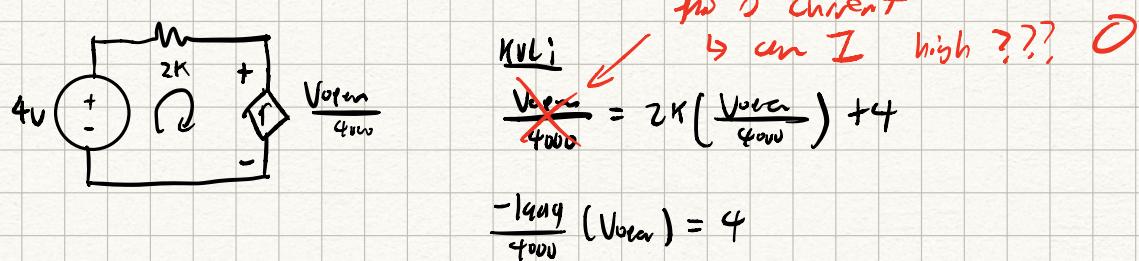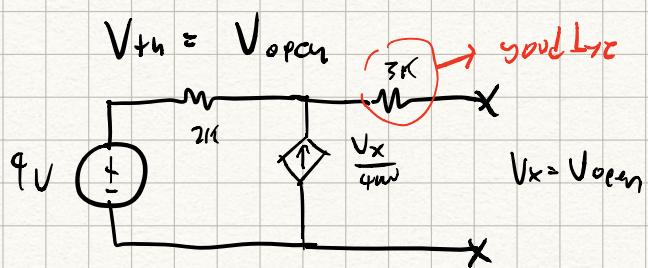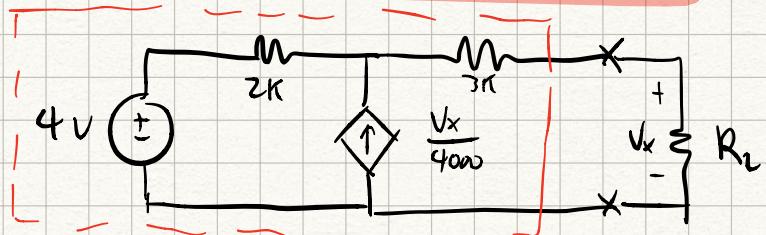What if you have independent and dependent sources?



$$\frac{V_{open}}{4000} = 2k \left(\frac{V_{open}}{4000} \right) + 4$$

$$-\frac{16k}{4000} (V_{open}) = 4$$

$$V_{open} = \frac{16k}{-16k} = -8V$$

$$4 = 2k_i + V_{open}$$

$$4 = 2k \left(-\frac{V_{open}}{4000} \right) + V_{open}$$

careful
sign

direction:


$$4 = -\frac{1}{2} V_{oc} + V_{oc}$$

$$4 = \frac{1}{2} V_{oc}$$

$$8V = V_{oc}$$



R_{th} ?

$$R_{th} = R_N = \frac{V_{oc}}{I_{sc}}$$

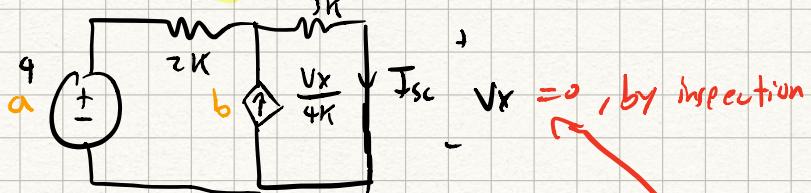

$V_x = 0$, by inspection

Superposition

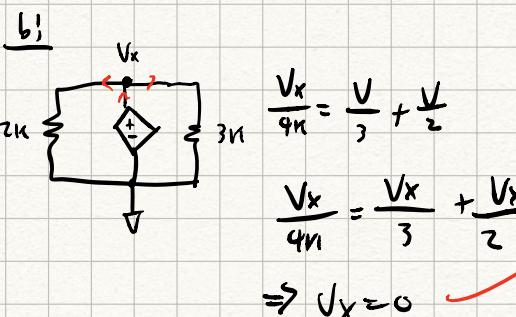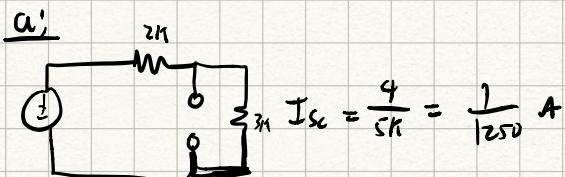

$$\therefore I_{sc} = \frac{1}{1250} A$$

$$R_{th} = R_N = \frac{V_{oc}}{I_{sc}} = 8(1250) = 10k \Omega$$

