

# AC POWER

## instantaneous power

$$p(t) = \frac{v^2(t)}{R} = v(t) \cdot i(t)$$

## average power

$$P_{av} = \frac{1}{T} \int_0^T p(t) dt$$

$$= \frac{1}{T} \int_0^T \frac{v^2(t)}{R} dt$$

$$= \frac{1}{R} \left( \sqrt{\frac{1}{T} \int_0^T v^2(t) dt} \right)^2$$

define  $V_{rms}$  as  $\sqrt{\frac{1}{T} \int_0^T v^2(t) dt}$

$$s_i \quad P_{av} = \frac{V_{rms}^2}{R}$$

$$\text{for sinusoids, } V_{rms} = \frac{V_p}{\sqrt{2}}$$


$$\text{from this, } I_{rms} = \frac{I_p}{\sqrt{2}}$$

## maximum power

Similar to DC, we first Thevenin-ize the circuit.

$$Z_{th} = R_{th} + X_{th} j$$

$$Z_L = R_L + X_L j$$

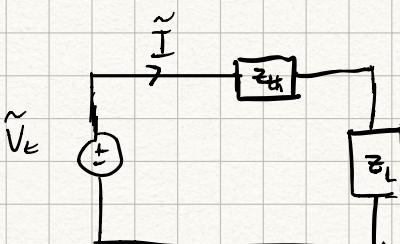

We know that maximum power is transferred when

$$R_{th} = R_L \quad \text{and} \quad X_L = -X_{th}$$

$$Z_L = R_{th} - jX_{th} \quad Z_L^* = Z_{th}$$

$$Z_L = Z^*_{th}$$

thus, if  $Z_{th}$  is inductive,  $Z_L$  is capacitive  
if  $Z_{th}$  is capacitive,  $Z_L$  is inductive

$$P_{max} = \frac{|V_{th}|^2}{8R_{th}}$$

### real power


if  $V(t) = V_m \cos(\omega t + \theta_v)$  and  
 $i(t) = I_m \cos(\omega t + \theta_i)$ ,

$$P(t) = V(t) \cdot i(t) = V_m I_m \cos(\omega t + \theta_v) \cos(\omega t + \theta_i)$$

$$\therefore \cos(a) \cos(b) = \frac{1}{2} [\cos(a-b) + \cos(a+b)],$$

$$P(t) = \frac{1}{2} V_m I_m [\underbrace{\cos(\theta_v - \theta_i)}_{\text{constant}} + \underbrace{\cos(2\omega t + \theta_v + \theta_i)}_{\text{time dependent w/ double angular freq.}}]$$

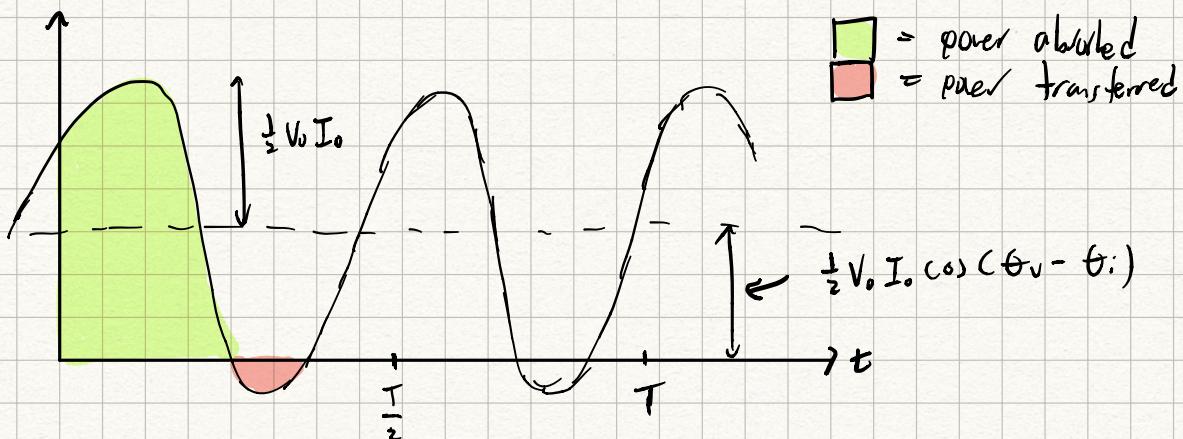instant power = constant + time dependent w/ double angular freq.



let;

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) \quad (\text{real/active power})$$

and

$$Q = \frac{1}{2} V_m I_m \sin(\theta_v - \theta_i) \quad (\text{reactive power})$$

$$p(t) = \frac{1}{2} V_m I_m [\cos(\theta_v - \theta_i) + \cos(2wt + \theta_v - \theta_i)]$$

$$\therefore \cos(\alpha + \beta) = \cos \alpha \cos \beta - \sin \alpha \sin \beta,$$

$$= \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) + \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) \cos(2wt) + \frac{1}{2} V_m I_m \sin(\theta_v - \theta_i) \sin(2wt)$$

$$= P + P \cos(2wt) + Q \sin(2wt)$$


Power factor

$$pf = \cos(\theta_v - \theta_i)$$

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) = \frac{1}{2} V_m \cdot I_m \cdot pf$$

$$\cdot a = cV$$

ex

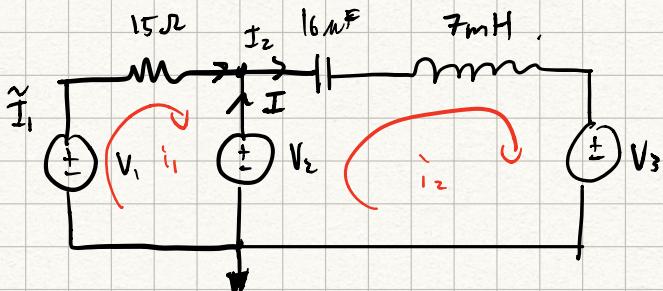

$$-V_2 + \frac{Q_c}{C} + L \frac{di}{dt} + V_3 = 0$$

$$+V_2 - V_3 - \frac{Q_c}{C} = L \frac{di}{dt}$$

$$I = \int 10 \cos(1000t + \frac{\pi}{2}) - 240 \cos(1000t - \frac{\pi}{2}) -$$

$$W = 1000$$

$$\tilde{V}_1 = 15 I_1 + \tilde{V}_2$$

$$Z_R = 15\Omega$$

$$V_2 = I_2(Z_1 + Z_2) + V_3$$

$$Z_C = -j \frac{1}{WC} = -j \frac{1}{1000(16 \times 10^{-6})}$$

$$I_1 = \frac{V_1 - V_2}{15}$$

$$Z_L = j \omega L = j(1000)(7 \times 10^{-3})$$

$$\rightarrow \tilde{V}_2 = 10 \angle 90^\circ$$

$$\tilde{V}_1 = 20 \angle 0^\circ$$

$$\rightarrow \tilde{V}_3 = 240 \angle -90^\circ \quad \leq I = i_2 - i_1$$

$$V_2 = 10 \angle 90^\circ$$

$$I_2 = \frac{V_2 - V_3}{L - 62.5j}$$

$$I_1 = \frac{4}{3} - \frac{2}{3}j$$

$$= 26.565^\circ$$

$$= -4.5045 A = 4.5045 \angle$$

$$pf = \cos(0 - 26.565^\circ) = 0.8944$$

$$\epsilon I = -4.5045 - \left( \frac{4}{3} - \frac{2}{3}j \right) = -5.17 - \frac{1}{3}j$$

$$\Rightarrow -176.31^\circ$$